

Παναγιώτης Κρεμμύδας 1435
1/19/2016

Lab exercise 4:

LCD component driver

CE430: Digital Circuits Lab

Electrical& Computer Engineering

University of Thessaly

Contents

0: Introduction

1: LCD Command Set modulation: Initialization sequence transmitted prior any instructions that establishes the four-bit interface to the LCD component and signal modulation for communicating through that interface

2: LCD Character Display Control: Sends commands to the LCD controller through the Command Set modulation module reading the appropriate blocks from the BRAM.

3: Challenges & Solutions in the designing, testing and implementing of the above

Introduction:

Implementation of a Liquid Crystal Display driver. The goal is to experiment with the various functions of the Spartan3E's onboard LCD.

The suggested sample string for testing the aforementioned driver is the typical message ABCDEFGHIJKLMNOPabcdefghijklmno , the last(32nd) character on the LCD being a clockwise rotating single digit cursor. The message is registered in the BRAM memory of the FPGA and the LCD driver is utilized to continuously drive it in the LCD refreshed in 1 second intervals (including the display of the rotating cursor implementation).

Placement of the BRAM should be preconfigured to take place in the uppermost left part of the available memory on the Spartan3E board.

FPGAs like the Spartan3E board typically have a preconfigured synthesizable processor to drive the LCD and make the implementation less complicated . Because the use of the above processor can utilize a big portion of the LUTs and registers of the FPGA, it can prohibit functionality or increase the hardware requirements of an FPGA implementation. This project involves direct implementation of some of the LCD driver's functions in the main system tailored for minimum footprint in the available resources.

Part 1 - LCD Command Set modulation:

Implementation

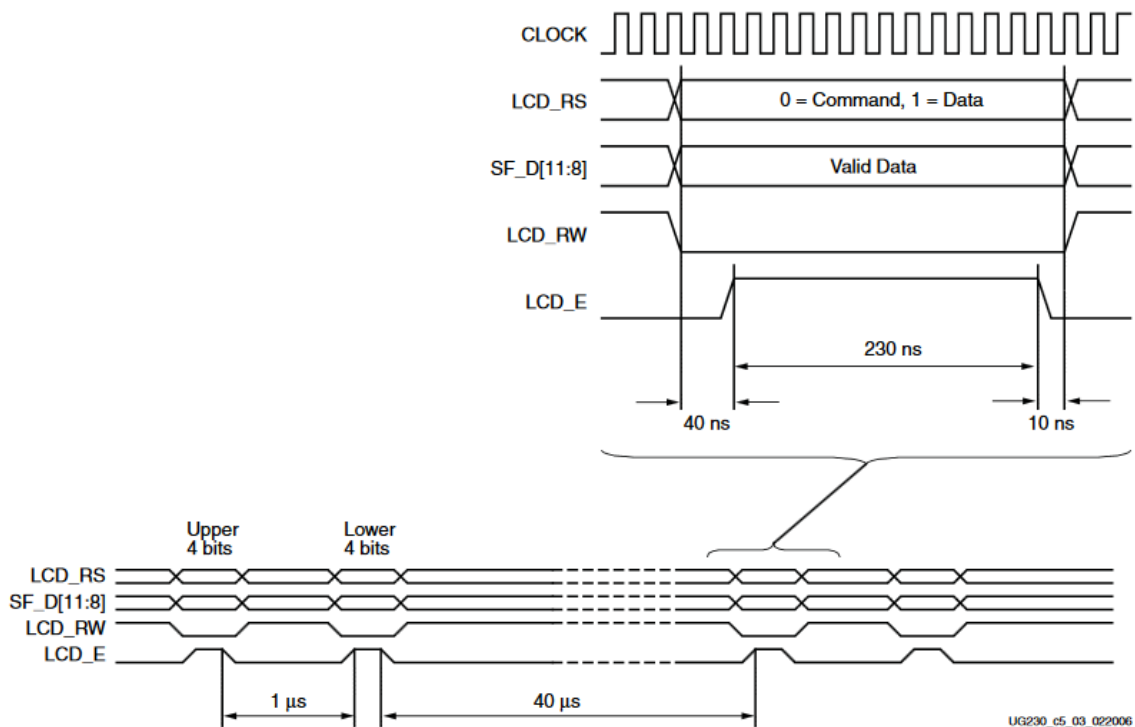


Figure 5-6: Character LCD Interface Timing

As shown in the above figure of the Xilinx Spartan3 manual write operations to the LCD are taking place by initializing the LCD_RS, LCD_RW, and SF_D[11:8] signals at least 40 ns before the LCD_E (enable signal) goes High. The LCD_E signal must remain High for 230 ns or longer. A power-on initialization sequence is transmitted prior any instructions. After the power-on initialization is completed, the four-bit interface is now established. The name of the module implementing the above is: Sync_10_bit_interface:

3state FSM:

DATA_INACTIVE: Communication interface remains inactive or performs the Power-On Initialization.

DATA_INITIALIZATION: initializing the LCD_RS, LCD_RW, and SF_D[11:8] signals according to the manufacturer's specified modulation

ENABLE_MODULATION_START: initializing the LCD_E signal according to the manufacturer's specified modulation

Waitingtime: Configures the following delays: 1us (transmission of the next 4bits), 40us (transmission of the next command), 15000us (display activation time), 1.64ms or 1s depending on the LCD_RS input (Clear Display or Display refresh period)


LCD_RW = 0; Display permanently accepts data in write mode. The LCD_RW signal can be tied Low permanently because the FPGA generally has no function in reading information in the current implementation.

next_command: Signals a posedge when next command transmission is available (implemented for partB)


Module data input: [10:0] UNMODULATED_DATA: { LCD_E , LCD_RS , LCD_RW=1'b0 , 8bit command set} In the current implementation LCD_E is 0 when running Clear Display or Display refresh functions. LCD_RS is 0 when not writing characters to the LCD screen and LCD_RW is always 0 because no characters are read using the LCD component.

https://github.com/kmd178/Digital_Systems_lab4_LCD/tree/1c6729b569a659d839f0b7cd28ae04cb531f7ad7


Verification

 


15ms: Delay for display activation

 

 1us: Delay for the next 4bit transmission



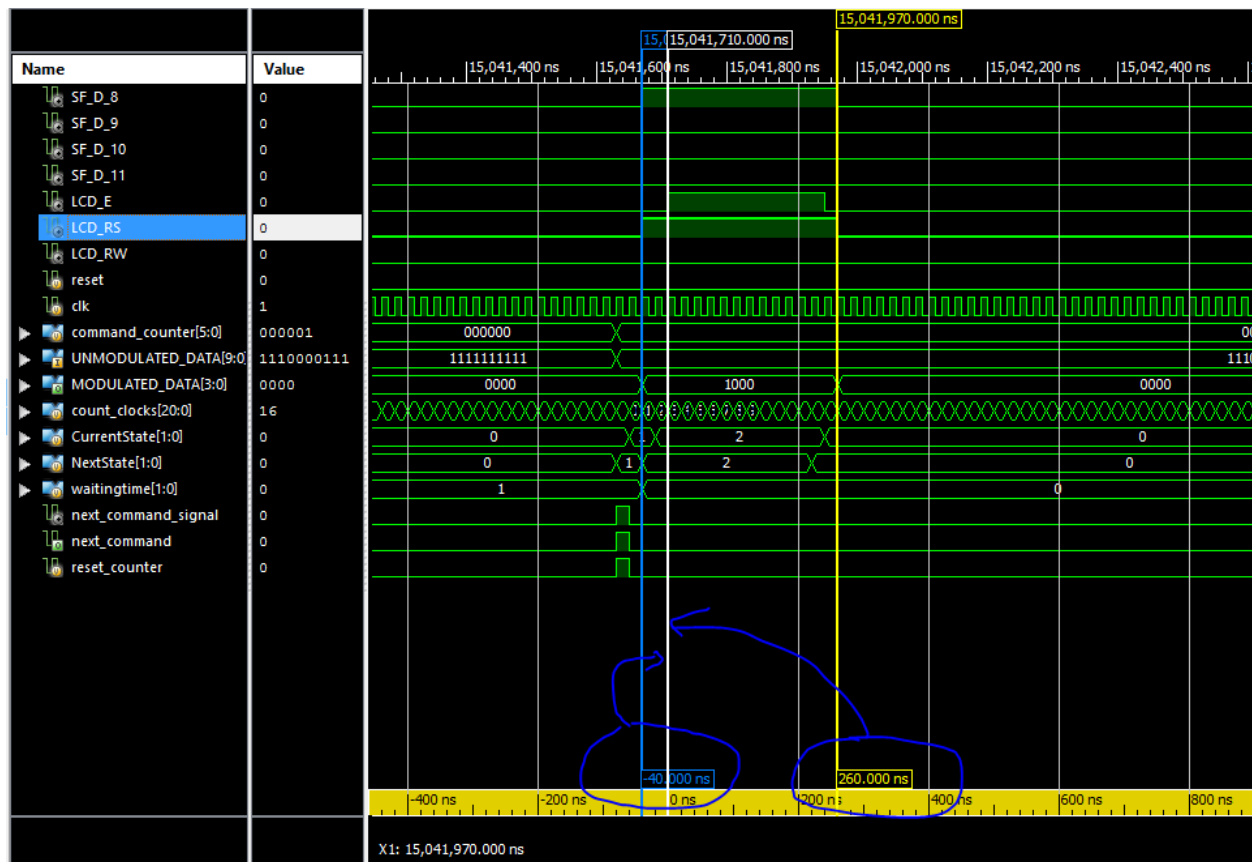40us: Delay for the next command transmission



40-240ns: Modulation of LCD_RS, LCD_RW, and SF_D[11:8], LCD_E signals

As indicated the corresponding output is assigned through the initialized memory. Output waveforms are performing as expected.

Experiment/Resulting implementation

FPGA board testing was not necessary for this part of the assignment

Part 2 - LCD Character Display Control:

Implementation

As shown in the Xilinx Spartan3 manual the following tables describe the commands available:

Function	LCD_RS	LCD_RW	Upper Nibble				Lower Nibble			
			DB7	DB6	DB5	DB4	DB3	DB2	DB1	DB0
Clear Display	0	0	0	0	0	0	0	0	0	1
Return Cursor Home	0	0	0	0	0	0	0	0	1	-
Entry Mode Set	0	0	0	0	0	0	0	1	I/D	S
Display On/Off	0	0	0	0	0	0	1	D	C	B
Cursor and Display Shift	0	0	0	0	0	1	S/C	R/L	-	-
Function Set	0	0	0	0	1	0	1	0	-	-
Set CG RAM Address	0	0	0	1	A5	A4	A3	A2	A1	A0
Set DD RAM Address	0	0	1	A6	A5	A4	A3	A2	A1	A0
Read Busy Flag and Address	0	1	BF	A6	A5	A4	A3	A2	A1	A0
Write Data to CG RAM or DD RAM	1	0	D7	D6	D5	D4	D3	D2	D1	D0
Read Data from CG RAM or DD RAM	1	1	D7	D6	D5	D4	D3	D2	D1	D0

Signal Name	FPGA Pin	Function	
SF_D<11>	M15	Data bit DB7	Shared with StrataFlash pins SF_D<11:8>
SF_D<10>	P17	Data bit DB6	
SF_D<9>	R16	Data bit DB5	
SF_D<8>	R15	Data bit DB4	
LCD_E	M18	Read/Write Enable Pulse 0: Disabled 1: Read/Write operation enabled	
LCD_RS	L18	Register Select 0: Instruction register during write operations. Busy Flash during read operations 1: Data for read or write operations	
LCD_RW	L17	Read/Write Control 0: WRITE, LCD accepts data 1: READ, LCD presents data	

Display Configuration is done with the following 4 commands that utilize the functions of the LCD through their specified parameters (Display characters stored in DD RAM, No cursor, Auto-increment address counter, Shifting disable, Clear Display).

Command counter: Increments by 1 every time a command finishes execution in the sync_10bit_interface module (Will increments 2, 3 or 4 depending for displaying the 32nd character according to the currently active iteration). The corresponding LCD_RS and LCD_E signals to the active commands are assigned in the lcd_controller module according to that counter. (a better implementation on different specifications would require 10 bit slots without character reading or 11 bit slots including the character reading function)

Function Set

Sets interface data length, number of display lines, and character font.

The Starter Kit board supports a single function set with value 0x28.

Execution Time: 40μs 00001010-- -> 0000101000 = 0x28

Entry Mode Set

Sets the cursor move direction and specifies whether or not to shift the display.

These operations are performed during data reads and writes.

Execution Time: 40μs //00000001-- -> 0000000110 = 0x06

Bit DB1: (I/D) Increment/Decrement

0 Auto-decrement address counter. Cursor/blink moves to left.

1 Auto-increment address counter. Cursor/blink moves to right.

Bit DB0: (S) Shift

0 Shifting disable

1During a DD RAM write operation, shift the entire display value in the direction controlled by Bit DB1 (I/D). Appears as though the cursor position remains constant and the display moves.

Display On/Off

Display is turned on or off, controlling all characters, cursor and cursor position character (underscore) blink.

Execution Time: 40µs 0000001--- -> 0000001100 = 0x0C

Bit DB2: (D) Display On/Off

0No characters displayed. However, data stored in DD RAM is retained

1Display characters stored in DD RAM

Bit DB1: (C) Cursor On/Off

0No cursor

1Display cursor

Bit DB0: (B) Cursor Blink On/Off

0No cursor blinking

1Cursor blinks on and off approximately every half second

Clear Display

Clear the display and return the cursor to the home position, the top-left corner.

This command writes a blank space (ASCII/ANSI character code 0x20) into all DD RAM addresses. The address counter is reset to 0, location 0x00 in DD RAM. Clears all option settings. The I/D control bit is set to 1 (increment address counter mode)

Execution Time: 82µs - 1.64 ms = 82.000 cycles. 0000000001 = 0x01

The following command set is stored into 8bit BRAM slots:

0:Function Set	0000101000	0x28	
1:Entry Mode Set	0000000110	0x06	
2:Display On/Off	0000001100	0x0C	
3:Clear Display	0000000001	0x01	
4: -Blank-	0000000000	0x00	Wait 1,64ms
5: CGRAM SET ADDRESS	0001 000 001	0x41	{rs,rw,7,6,5,4,3,2,1,0}
6: INSERT " ^ "	1000011111	0x1F	
7: CGRAM SET ADDRESS	0001 001 001	0x49	//Implemented on the hypothesis that every WRITE CHAR will iterate CGRAM Memory address by 1 (meaning next row on the 5x8bitmap)
8: INSERT " "	1000010000	0x10	
9: INSERT " "	1000010000	0x10	
10: INSERT " "	1000010000	0x10	
11: INSERT " "	1000010000	0x10	
12: INSERT " "	1000010000	0x10	
13: CGRAM SET ADDRESS	0001 010 110	0x56	
14: INSERT " _ "	1000011111	0x1F	


```


15: CGRAM SET  ADDRESS 0001 011 001                0x59
16: INSERT "| "                1000000001          0x01
17: INSERT "| "                1000000001          0x01
18: INSERT "| "                1000000001          0x01
19: INSERT "| "                1000000001          0x01
20: INSERT "| "                1000000001          0x01

21: DDRAM SET  ADDRESS 001 0000000 {rs,rw,7,6,5,4,3,2,1,0} rs=0 0x80
...
22-37: WRITE CHAR ON THE SPECIFIED ADDRESS (+ITERATION)    rs=1 0x41 until 0x50
...
38: DDRAM SET  ADDRESS 001 0111111 {rs,rw,7,6,5,4,3,2,1,0} rs=0 0xC0
...
39-53: WRITE CHAR ON THE SPECIFIED ADDRESS rs=1 0x61 until 0x6F
...
54-57: WRITE CHAR (rotationally every 1 second loop) rs=1 0x00 or 0x01 or 0x02 or 0x03
58: -Blank-  00000000 Wait 1 second and repeat from 21st command


```

https://github.com/kmd178/Digital_Systems_lab4_LCD/tree/96d0798722fa253aad8cf551160a57209614bffb


Verification

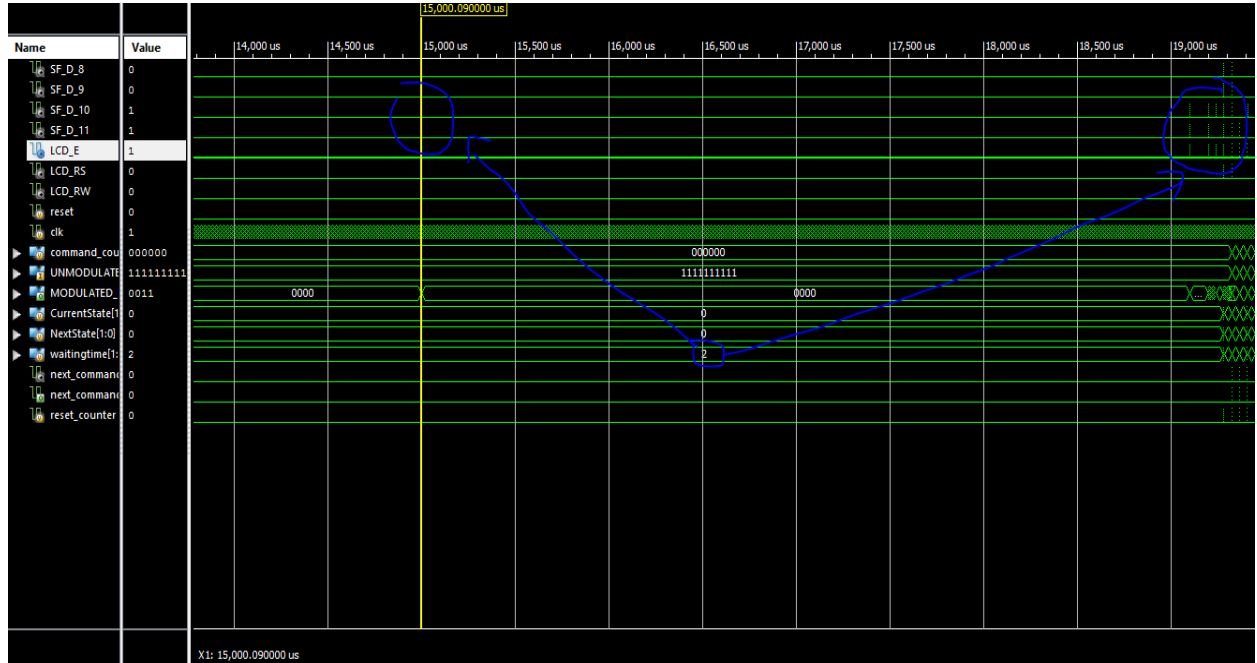

Initialization modulation

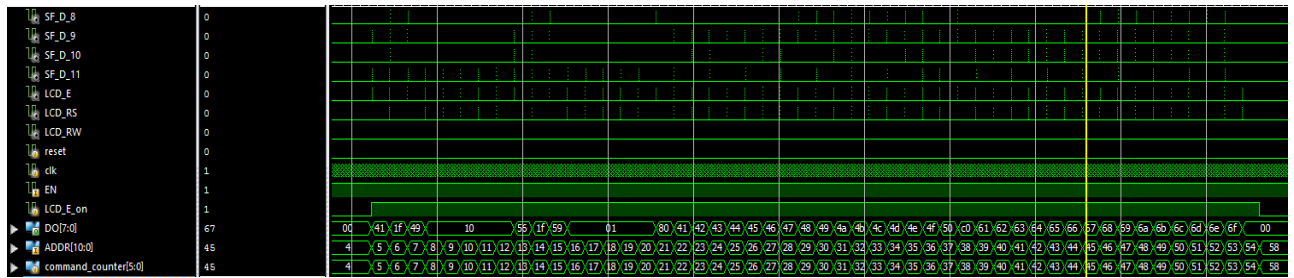


Instruction set

 

Instruction set for the 1second intervals

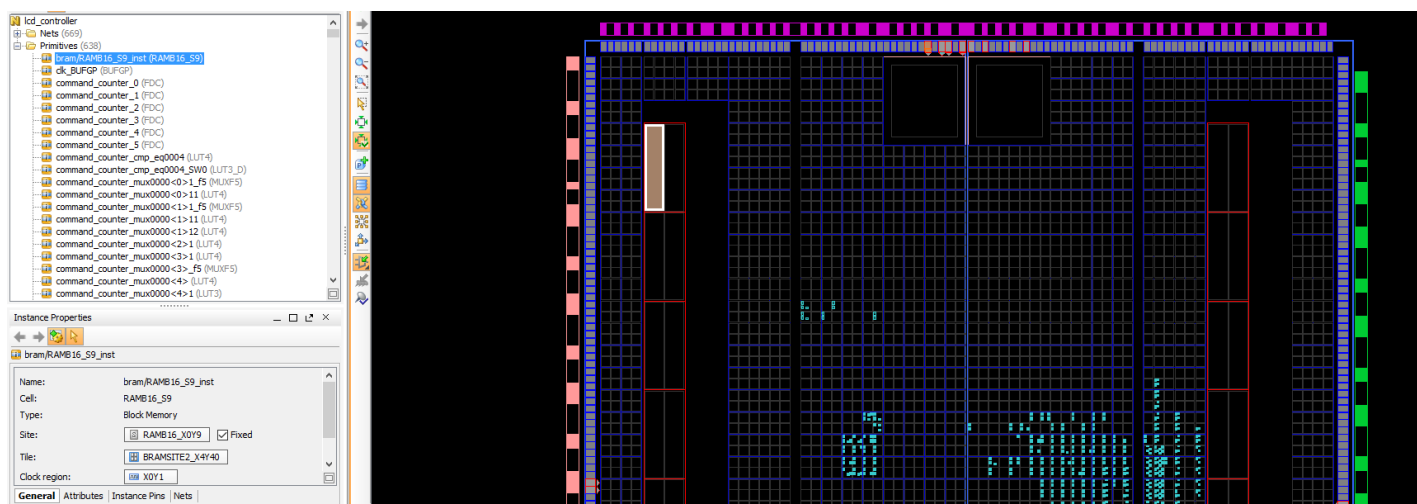Output waveforms are performing as expected.



BRAM placement configured to take place in the uppermost left part of the available memory on the Spartan3E board as indicated.

Experiment/Resulting implementation

First trial: LCD displaying unrecognizable characters

Second trial: Implementation without displaying characters or assigning bitmap data to the CGRAM resulted in a similar behavior

Third trial: Implementation without using SET ADDRESS commands 0x80 or 0xC0 gave expected results.

The configuration is set to display the message "ABCDE " rotationally refreshing in 1 second intervals. (The driver keeps writing data on the DDRAM until its address counter iterates to the beginning where it displays the data written again while going through the 0x00 to 0x0F and 0x40 to 0x4F memory addresses.)

Challenges & Solutions:

DDRAM SET ADDRESS 001 xxxxxxx {rs,rw,7,6,5,4,3,2,1,0} was not performing as expected in the supplied SPARTAN3E board . Probable causes can be hardware misimplementation or malfunction or misinterpretation of the board's documentation.

The problem above is clear using a different command set implementation where Command 0x81 does not set the DDRAM address to 1 as expected but causes errant behavior.

Command set written reverse:

00_00_34_33_32_31_30_45_44_43_42_41_81_20_00_01_0C_06_28

https://github.com/kmd178/Digital_Systems_lab4_LCD/tree/fd10a6c63f158b86f32e481b33aea53895201bdf

The third trial was succesful using the implementation below:

Command set written reverse:

(continuing)_43_42_41_20_45_44_43_42_41_20_20_00_01_0C_06_28

https://github.com/kmd178/Digital_Systems_lab4_LCD/tree/b895f2dc0feb562ca4ec983b583abb145a07629f